

S.B. Roll No.....

POWER ELECTRONICS
4th Exam/ECE/ETV/ECE-II/6128/2961/Nov'18

Duration: 3Hrs.

M.Marks:75

SECTION-A

Q1. Do as directed.

15x1=15

- a. An SCR contain _____ PN junctions.
- b. An UJT is a _____ device.
- c. A TRIAC can conduct in _____ directions.
- d. The value of firing angle cannot be more than _____.
- e. Full wave rectifier allows power flow in both directions (T/F).
- f. GTO can be turned off by _____ gate signal.
- g. Power rating of UPS is given in _____.
- h. GTO stands for _____.
- i. Three Types of UPS are _____, _____ and _____.
- j. An inverter converts _____.
- k. In normal operation, anode of SCR is kept _____ w. r. t cathode.
- l. Dual converter can be operated in _____ quadrants.
- m. Commutation can be classified as _____ and forced commutation.
- n. A UJT after reaching the valley point goes to its saturation state. (T/F).
- o. The series inverters are also known as _____ commutated inverters.

SECTION-B

Q2. Attempt any five questions.

5x6=30

- i. What are the different applications of UPS system?
- ii. Explain working principle of inverter circuit with the help of block diagram.
- iii. Explain any three methods of SCR triggering.
- iv. What do you mean by heat sink? What is the necessity of heat sink?
- v. Write difference between ON line And OFF line UPS system
- vi. Draw and explain block diagram of dual converter.
- vii. How SCR work as Switch?
- viii. Write advantages and disadvantages of HVDC transmission system.

SECTION-C

Q3. Attempt any three questions.

3x10=30

- a. Explain the operation of UJT with the help of characteristics.
- b. Write short note on the following. **(any two)**
 - i. Gate turn off thyristor (GTO).
 - ii. Cyclo converter.
 - iii. Chopper.
- c. Explain construction and working of SCR & draw its V-I characteristics. List some applications of SCR.
- d. Describe the working of single phase full wave centre tap rectifier with the help of wave forms and circuit diagram.
- e. Explain the working principle of parallel inverter with the help of circuit diagram.