

S.B.Roll No.....

**Network Filters And Transmission Lines**

**4<sup>th</sup> Exam/ECE/EMP/ETV/ECE(II)6107/2261/May'15**

**Duration :3hrs**

**Max Marks:75**

**SECTION –A**

**Q.1. Fill in the blanks:**

**(1.5 x 10=15)**

- (a) A network is said to be non-linear if it does not satisfy .....
- (b) The standing wave ratio is equal to ..... When the load is perfectly matched.
- (c) The shunt element of a band stop filter is .....
- (d) For a prototype high pass filter with design resistance  $R_0$  and cut off frequency  $f_c$ , the capacitance  $C$  is given by .....
- (e) In a lattice network if diagonal impedances are alike and identical as well series impedance, the network will be.....
- (f) In high pass butter worth filter  $V_o = \dots\dots\dots * E_i$ .
- (g) h-parameter in term of Y-parameters are  $h_{11} = \dots\dots\dots$ ,  $h_{12} = \dots\dots\dots$ ,  $h_{21} = \dots\dots\dots$  .
- (h) Output impedance  $Z_o$  in term Of Z-parameter is  $= \dots\dots\dots$  .
- (i) Wave length and phase velocity are related as .....
- (j) Frequency of infinite attenuation is .....

**SECTION –B**

**Q.2 Note : Attempt any five questions:**

**(5 x 6=30)**

- a. Discuss the properties of crystal filter.
- b. Discuss the various types of transmission lines.
- c. Design a prototype section of band pass filter with diagram
- d. Explain the application of transmission lines.
- e. Discuss limitations of passive filters
- f. Distinguish between balanced and unbalanced attenuators.
- g. Derive parameters of two port network.

**SECTION –C**

**Note : Attempt any three questions:**

**(10 x 3=30)**

**Q.3**

- (a) What do you mean by symmetrical network ?
- (b) Explain the concept and significance of characteristic impedance .

**Q.4** Write a short note on :

- (a) Propagation constant of a transmission line.
- (b) Voltage standing wave Ratio.

**Q.5** Derive the equations of attenuation constant, phase constant and propagation constant.

**Q.6** Differentiate between active and passive filter