

S.B. Roll No.....

**NETWORK FILTER AND TRANSMISSION LINES**  
**4<sup>TH</sup> Exam /ECE/ETV/EMP/ECE II/6107/2261/Nov'16**

**Duration: 3hrs.**

**M.Marks: 75**

**SECTION: A**

**Q.1 Do as directed:**

**1.5x10=15**

- a) Propagation constant term is used in \_\_\_\_\_.
- b) A two port network may have \_\_\_\_\_ and \_\_\_\_\_ elements.
- c) Attenuators are used to \_\_\_\_\_ the voltage, current or power.
- d) Variable attenuators have constant \_\_\_\_\_ and \_\_\_\_\_ impedances.
- e) A line works as \_\_\_\_\_ filter.
- f) The characteristics impedance of distortion less line is \_\_\_\_\_.
- g) In a transmission line, VSWR is a \_\_\_\_\_ quantity.
- h) Butterworth filter has \_\_\_\_\_ response.
- i) For high pass filters, pass band extends upto \_\_\_\_\_.
- j) \_\_\_\_\_ attenuator is used as volume control in communication receiver.

**SECTION: B**

**Q.2 Attempt any five questions:**

**5x6=30**

- a) Explain different losses in a transmission line.
- b) Derive the relationship between decibel and Neper.
- c) Discuss in brief butter worth filter.
- d) Define the terms  
(i) Propagation constant (ii) Attenuation constant (iii) Phase shift constant
- e) Write short note on insertion loss.
- f) What is phase constant of two port network?
- g) Derive an expression for open and short circuit impedance of half section.
- h) How is a line represented by a T-circuit? Derive an expression for its characteristic impedance.

**SECTION: C**

**Q.3 Attempt any three questions:**

**3x10=30**

- a) (i) Differentiate between one port network and two port network.  
(ii) What are the properties of asymmetrical network?
- b) (i) Discuss the operation of symmetrical bridge T-type attenuator.  
(ii) Discuss the concept of ladder attenuator.
- c) Explain the concept of working of Low Pass and High pass filters and band pass filters.
- d) Derive an expression for characteristics impedance using  $\pi$  type network circuit for transmission line.