

S.B. Roll No.....

**POWER ELECTRONICS**

4<sup>th</sup> Exam/ECE/6128/June'15

**Duration : 3 hrs.**

**M. Marks: 75**

**Question No. 1 is compulsory.**

1.5x10=15

**Section-A**

- Q.1
- (a) A device that can not be triggered with voltage or either polarity.....
  - (b) Holding current is ..... latching current.
  - (c) A GTO is a .....controlled device.
  - (d) Speed of AC drives can be controlled by.....
  - (e) ..... UPS also called double conversion UPS.
  - (f) Cyclo converter drives are generally employed in.....
  - (g) In half wave rectifiers, one switching device is used. (T & F)
  - (h) Full wave rectifiers allow power flow in both directions. (T & F)
  - (i) SCR is used in the speed control of a DC motor. (T & F)
  - (j) UJT is a device that does not exhibit negative resistance characteristic (T & F)

**Section-B**

Q 2. **Attempt any six questions:** 5x6

- (i) Explain the working principle of DIAC.
- (ii) Explain role of heat sink in power devices.
- (iii) What is an inverter? List a few industrial applications of inverters.
- (iv) Write short note on slip power control of AC drives.
- (v) Explain working of UJT as a relaxation oscillator.
- (vi) Draw the symbol of diac and its characteristic.
- (vii) What do you mean by class B chopper? Explain.
- (viii) Explain why natural commutation is not possible in d.c. circuits?

**Section-C**

Q 3. **Attempt any three questions :** 10x3

- (a) Write short note on any two of the following:
  - (i) UPS
  - (ii) SMPS
  - (iii) AC drive
- (b) Explain with the help of circuit diagram, the working principle of a single phase series inverter.
- (c) Explain Phase control, Constant V/F operation and Cyclo converter/inverter drives with reference to AC drive control.
- (d) Explain the working of 3 phase half wave controlled rectifier.
- (e) Explain the specification of a thyristor.