

S.B. Roll No.....

ELECTRONICS-I
3rd Exam/Elect/0525/May'18

Duration: 3Hrs.

M.Marks:75

SECTION-A

Q1. Fill in the blanks.

10x1.5=15

- a. In P-type semiconductors, the minority carriers are _____
- b. A MOSFET has _____ terminals.
- c. An ideal Voltage source has _____ internal resistance.
- d. Zener diode is made to operate in _____ region.
- e. In a transistor, base is made very _____.
- f. The three terminals of a transistor are _____ base and _____
- g. The polarity of diode terminals can be checked by _____
- h. A single stage amplifier contains _____ transistors
- i. In an amplifier, power gain= current gain * _____ gain
- j. For power amplification mostly _____ coupling is used.

SECTION-B

Q2. Attempt any five questions.

5x6=30

- i. Explain what you mean by constant current source.
- ii. What is a transformer? Mention important applications of transformer.
- iii. What is a tunnel diode? Draw its symbol and explain its Characteristics.
- iv. What do you mean by h-parameters of transistor? Explain.
- v. Explain with suitable diagram intrinsic and extrinsic semiconductors.
- vi. Differentiate between dc and ac load line.
- vii. Explain the term biasing. Why a transistor should be biased?

SECTION-C

Q3. Attempt any three questions.

3x10=30

- a. Draw the circuit diagram of transformer coupled amplifier and explain its working and frequency response.
- b. Explain the output characteristics of CE transistor. Indicate the three operating regions over it.
- c. With the help of diagram and waveform, explain the working of full wave bridge rectifier. Also write its advantages and disadvantages.
- d. Draw construction details of JFET and explain why FET is called voltage controlled device?
- e. Describe the following filter circuits
 - i. Shunt capacitor filter
 - ii. Series inductor filter
 - iii. Choke input LC filter