

S.B. Roll No.....

**DIGITAL ELECTRONIC AND MICROPROCESSORS**  
**5<sup>th</sup>/Elect./2529/Nov'15**

**Duration: 3hrs.**

**M.Marks=75**

**SECTION-A**

**Q 1. Fill in the blanks:**

**10x1.5=15**

- (i) RAM stands for.....
- (ii)  $X+X=$ .....
- (iii) The ..... language uses strings of 0's and 1's.
- (iv) 2's complement of 11101 is .....
- (v) If both inputs of XOR gate are high, the output is.....
- (vi) The Boolean expression  $(A+C')(B'+C')$  simplifies to .....
- (vii) A half adder consists of ..... gate and .....gate
- (viii) Flip flop is a ..... Circuit.
- (ix) A typical value of conversion time for A/D converter may be about.....
- (x) A program written in mnemonics is called..... program.

**SECTION-B**

**Q 2. Attempt any SIX questions:**

**5x6=30**

- (i) What do you mean by interrupts? Discuss various hardware interrupts of 8085.
- (ii) (a) Perform BCD addition  
01100111 and 01010011  
(b) Differentiate b/w combinational and sequential circuits.
- (iii) Explain universal property of NAND gate.
- (iv) Discuss De Morgan's theorems with suitable examples.
- (v) Write short notes on various display devices.
- (vi) Discuss various types of shift registers.
- (vii) How race around condition can be eliminated in JK flip flop?
- (viii) Explain how semiconductor memories are classified on the basis of their working?

**SECTION-C**

**Attempt any THREE questions:**

**3x10=30**

- Q3.** (a) Explain Pin diagram of 8085.  
(b) What are the various addressing modes of 8085?  
(c) Instruction set of 8085
- Q4.** What do you mean by D/A converter? Explain Successive Approximation A/D converter.
- Q5.** (a) What is full adder? Explain with truth table and circuit diagram.  
(b) With neat diagram, explain octal to binary encoder.
- Q6.** (a) Draw logic symbol of SR flip flop and explain its working..  
(b) Design 4 bit Ring counter.
- Q7.** (a) Explain DMA scheme with flow chart.  
(b) By giving suitable examples, explain binary subtraction using 2's complement method.