

DIGITAL ELECTRONOICS

3rd Exam/ECE/Comp/IT/ETV/EMP/EEE/0262/0620/May 2015

Duration : 3hrs

M.marks: 75

Section-A

Q1. Fill in the blanks :

1x15

- (a) A train of pulses is signal.
- (b) Redix of actal no. Is
- (c) BCD stands for
- (d) ASCII code is abit code .
- (e) ECL stands for
- (f) Statement of associative law is.....
- (g) Boolean expression $D=A+\overline{B+C}$ is equal to gate .
- (h) Half adder is also known asgate
- (i) Multiplexer is also known as
- (j) A flip flop is a memory element. (true /false)
- (k) Module od 4 bit counter is
- (l) SIPO stand for
- (m)The fastest A/D conveter is
- (n) IC 7400 isgate
- (o) In k-map an octal eleminates variables .

Section –B

6x5

Note : Attempt any 5 questions :

- Q.2. i. Convert $(32)_5 = (?)_3$ MULTIPLY $(15)_{10} \times (8)_{16}$
- ii. What is parity , How can you detect errors using parity ?
 - iii. Explain universal gates with diagrams.?
 - iv. Draw the following expression $Y=\overline{C} + \overline{B}\overline{D} + A\overline{D}$ using Nand gate ?
 - v. Define Half substractor ?
 - vi. What are the basic difference MUX and DEMUX?
 - vii. Explain the function of JK flip flop ?

Section –C

10x3

Note : Attempt any three questions :

- Q3 Explain synchronous Decode counter ?
- Q4 (a) Explain tristate buffer ?
(b) Application of shift register ?
- Q5 (a) Explain full adder ?
(b) Explain 4 bits adder ?
- Q6 Simply four variable function using K-map and draw the circuit
 $F=\sum m(0, 4, 12, 8, 9, 13, 7, 15)$
- Q7 (a) What is multiplexer? Draw a logic diagram of 4:1 multiplexer?
(b) What is race round condition? how can it be avoided?