

S.B. Roll No.....

ELECTRONICS-I
3rd Exam/Elect/0525/Nov'18

Duration: 3Hrs.

M.Marks:75

SECTION-A

Q1. Fill in the blanks.

15x1=15

- a. The electronic components which cannot process the signal are called _____.
- b. The process of adding impurities in intrinsic semiconductor material is called _____.
- c. Resistivity of a semiconductor lies between _____.
- d. The value of knee voltage for silicon diode is _____ volts.
- e. An ideal diode has _____ reverse resistance.
- f. A zener diode is always operated in the _____ region.
- g. _____ Diode has a negative resistance.
- h. In a transistor, there are _____ pn junctions.
- i. The emitter of a transistor is doped _____.
- j. The biasing circuit which gives best stability to the Q point is _____.
- k. The ideal value of stability factor is _____.
- l. A transistor with its associated circuitry for amplification is called a _____.
- m. In an amplifier, power gain = current gain x _____ gain.
- n. The point at which DC and AC load lines interact each other is called _____.
- o. A FET has three terminals namely; source, drain and _____.

SECTION-B

Q2. Attempt any five questions.

5x6=30

- i. What are practical and ideal current and voltage sources?
- ii. List the main differences between intrinsic and extrinsic semiconductors?
- iii. Draw and explain V-I characteristics of P-N junction diode.
- iv. What is the use of filter circuit? List different types of filters.
- v. What do you mean by Saturation, Cut-off and Active regions?
- vi. What are different types of couplings used in transistor amplifier?
- vii. Write advantages and disadvantages of FET.

SECTION-C

Q3. Attempt any three questions.

3x10=30

- a. With the help of circuit diagram and waveforms, explain the functioning of a full-wave rectifier.
- b. Explain zener diode, its characteristics and applications.
- c. Draw and explain the circuit of common-emitter configuration of transistor and its characteristics.
- d. Describe the construction, operation and characteristics of FET with suitable diagrams.