

S.B. Roll No.....

INDUSTRIAL ELECTRONICS AND CONTROL OF DRIVES
5th Exam/Elect/EEE/2528/Nov'18

Duration: 3Hrs.

M.Marks:75

SECTION-A

Q1. Fill in the blanks.

15x1=15

- a. The numbers of PN junctions in a UJT are _____.
- b. Dual converters can be used to achieve _____ braking.
- c. The main application of cyclo converter circuit is found in _____ traction.
- d. For wide speed control _____ drives are used.
- e. In a thyristor holding current is less than _____.
- f. SCR stands for _____.
- g. Maintenance cost of electric control system is _____ in comparison to conventional systems.
- h. The efficiency of full wave rectifier is always _____ than the efficiency of half wave rectifier.
- i. The three terminals of SCR are known as _____.
- j. A device which converts dc power into ac power at desired voltage and frequency is called _____.
- k. A cyclo converter converts input power at one frequency to _____.
- l. A diac is used to trigger _____.
- m. SCRs are connected in parallel to enhance _____.
- n. In class E chopper can operate in _____ quadrants.
- o. The power rating of a UPS is given in _____.

SECTION-B

Q2. Attempt any six questions.

6x5=30

- i. Explain the working of single phase full wave controlled rectifier using a centre tapped transformer feeding RL load.
- ii. What is commutation? Discuss different types of commutation.
- iii. Draw and explain V-I characteristics of an SCR.
- iv. What do you understand by back up time of a UPS? What are the factors which can increase back up time?
- v. Differentiate between steps up and step down chopper.
- vi. Why a dual converter is called so?
- vii. Explain briefly the speed control of a dc series motor using chopper.
- viii. What are the main advantages of ac drives over dc drives?

SECTION-C

Q3. Attempt any three questions.

3x10=30

- a. What are the different methods of triggering SCR?
- b. What is cyclo converter? Explain with the help of a circuit diagram a single phase cyclo converter using centre tapped transformer.
- c. Explain the advantages and disadvantages of HVDC transmission system
- d. i) Why a heat sink is required with a thyristor?
ii) Why a freewheeling diode is called so?
- e. i) Draw and explain the working of a full wave single phase half controlled bridge rectifier.
ii) Write short notes on care and maintenance of lead acid battery.