

S.B. Roll No.....

## DIGITAL SYSTEM DESIGN

5<sup>th</sup>/EMP/0640/Nov'15

Duration 3 Hrs

M.Marks=75

### SECTION A

#### Q1. Do as directed

10x1.5=15

- I. S/N ratio stands for \_\_\_\_\_
- II. SSI stands for \_\_\_\_\_
- III. Expand BCD?
- IV. Flip-flop is a \_\_\_\_\_
- V. Who defined the Boolean algebra?
- VI. Why D flip flop is called so?
- VII. Define clock.
- VIII. Write the names of any two sequential circuits.
- IX. Draw NOT gate using NAND gate.
- X. Write the truth table of T flip flop?

### SECTION B

#### Q2. Attempt any FIVE Questions

5x6=30

- I. Design Full adder.
- II. Explain the different types of transmission media for interfacing with digital systems.
- III. How we can remove race round conditions?
- IV. What is the difference between synchronous and asynchronous sequential circuits?
- V. Discuss the spectrum analysis of analog signals.
- VI. Explain JK flip flop with truth table.
- VII. Discuss the hazards in details.

### SECTION C

#### Q3. Attempt any THREE questions:

3x10=30

- I. What are the various High Frequency problems in digital systems?
- II. Explain the Mealy and Moore Machines.
- III. Draw & explain the Universal Shift Register.
- IV. Write a note on: PAL, PLA & ROM.
- V. Design AND, OR & NOT gate using Universal gates.