

S.B. Roll No.....

DIGITAL ELECTRONICS

3RD Exam/ECE/ECE-II/ETV/CSE/COMP/IT/EEE/0620/Nov'18

Duration: 3Hrs.

M.Marks:75

SECTION-A

Q1. Fill in the blanks.

15x1=15

- a. In a digital system, digital signal requires _____ channel bandwidth.
- b. Collection of 4 bits is called _____.
- c. Radix of octal number is _____.
- d. BCD numbers express each decimal digit as a _____.
- e. TTL stands for _____.
- f. An inverter is also known as _____.
- g. The XOR gate is sometimes referred to as _____.
- h. LSI & VLSI devices use _____ technology.
- i. A multiplexer changes _____ data into _____ data.
- j. To overcome race around condition _____ type of flip flop is used.
- k. A ripple counter is _____ sequential circuit.
- l. IC 74194 is _____ shift register.
- m. The fastest A/D Converter is _____.
- n. Draw symbol of XNOR.
- o. The 2's complement of 11001000 is _____.

SECTION-B

Q2. Attempt any six questions.

6x5=30

- i. Convert each binary number to decimal
 - a) $(110011.11)_2$
 - b) $(101010.01)_2$
 - c) $(1000001.11)_2$
- ii. Explain ASCII code and convert a binary 1001011 to gray code.
- iii. What are the different error detection and correction codes?
- iv. Discuss the characteristics of TTL Logic Family.
- v. Explain the laws related to Boolean algebra.
- vi. Explain De Morgan's theorems.
- vii. Difference between Combinational and Sequential Circuit.
- viii. Design 4 bit ring counter.

SECTION-C

Note: Attempt any three questions.

3x10=30

Q3. Explain the universal property of NAND & NOR Gate.

Q4. Draw the Karnaugh Map for the following of four variables

- i. $F(A,B,C,D)=\sum m(0,1,2,3,4,5,10,11)$
- ii. $F(A,B,C,D)=\sum m(2,3,6,7,10,11,14,15)$

Q5. Write a short note on the following. **(any two)**

- a) Half Adder
- b) DEMUX
- c) Dual slope A/D Converter.

Q6. Explain the working principle of JK Master/ Slave flip flop and its truth table.

Q7. Explain Serial to Parallel Shift Register.